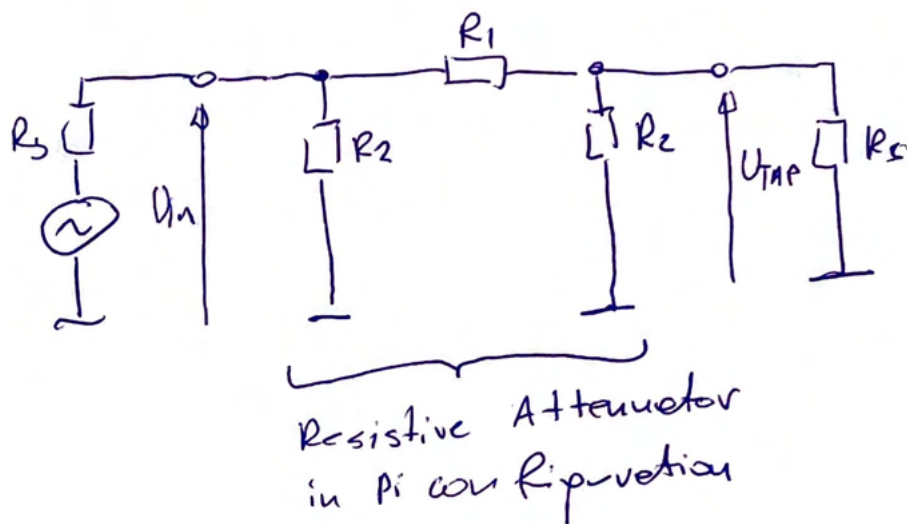


Principles of Operation

$$R_{S_{nominal1}} = R_{S_{nominal2}} = R_S = 50 \Omega$$

$$R_{1a} + R_{1b} + R_{1c} = R_1$$

Simplified circuit:



A_v - voltage attenuation

$$A_v = \frac{U_{out}}{U_{in}}$$

A_{dB} - attenuation expressed in dB

If we assume voltage attenuation $A_v = \frac{1}{100}$ then

$$A_{dB} = 20 \log(0,01) = 20 \log 10^{-2} = 20 \cdot (-2) = -40 \text{ dB}$$

Using formulas derived in [2] we can calculate resistor values:

$$R_2 = \left[\frac{1+A_v}{1-A_v} \right] \cdot R_S = \frac{1+0,01}{1-0,01} \cdot 50 = \frac{1,01}{0,99} \cdot 50 = \underline{\underline{51 \Omega}}$$

$$R_1 = \frac{(1-A_v^2)}{2 \cdot A_v} \cdot R_S = \frac{(1-0,01^2)}{2 \cdot 0,01} \cdot 50 = \frac{0,9999}{0,02} \cdot 50 = \underline{\underline{2500 \Omega}}$$

R_1 can be expressed in sum of standard resistor values.

Good approximation is: ~~820~~ 820 + 820 + 820 Ω or

820 + 820 Ω and 1k potentiometer.